

EE105 Lab Experiments

Prelab 9: MOS Characterization and Amplifiers

Solutions


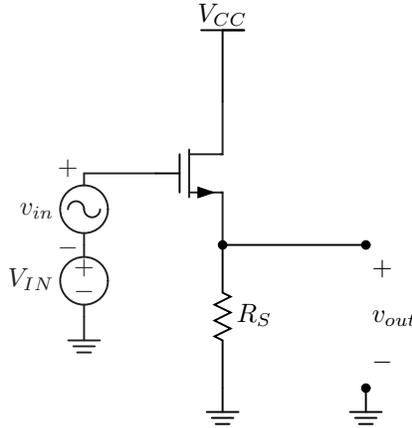


Figure 1: Common drain amplifier

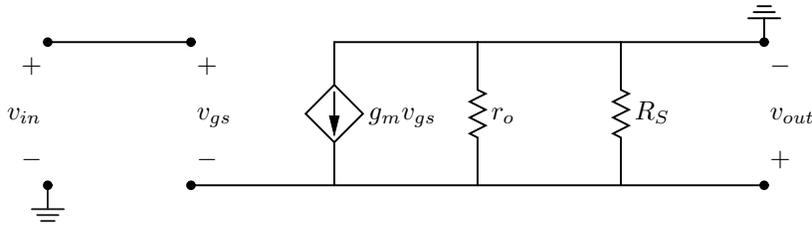1. Draw the small signal model for the common drain shown in Figure 1.



2. Derive the output impedance.

We short the input and apply a test source at the output.

$$\begin{aligned}
 v_t &= -v_{gs} \\
 g_m v_{gs} - \frac{v_t}{r_o \parallel R_S} + i_t &= 0 \\
 v_t \left(g_m + \frac{1}{r_o \parallel R_S} \right) &= i_t \\
 R_{out} = \frac{v_t}{i_t} &= \boxed{\frac{1}{g_m + \frac{1}{r_o \parallel R_S}}}
 \end{aligned}$$

3. Derive the voltage gain.

$$\begin{aligned}
 v_{out} &= g_m v_{gs} (r_o \parallel R_S) \\
 v_{in} &= v_{out} + v_{gs} \\
 v_{out} &= g_m (v_{in} - v_{out}) (r_o \parallel R_S) \\
 v_{out} (1 + g_m (r_o \parallel R_S)) &= g_m v_{in} (r_o \parallel R_S) \\
 A_v = \frac{v_{out}}{v_{in}} &= \boxed{\frac{g_m (r_o \parallel R_S)}{1 + g_m (r_o \parallel R_S)}}
 \end{aligned}$$

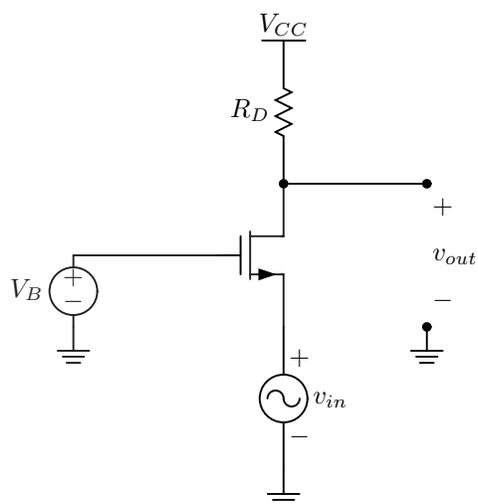



Figure 2: Common gate amplifier

4. Draw the small signal model for the common gate shown in Figure 2.

5. Derive the output impedance.

$$R_{out} = \boxed{r_o \parallel R_D}$$

6. Derive the voltage gain.

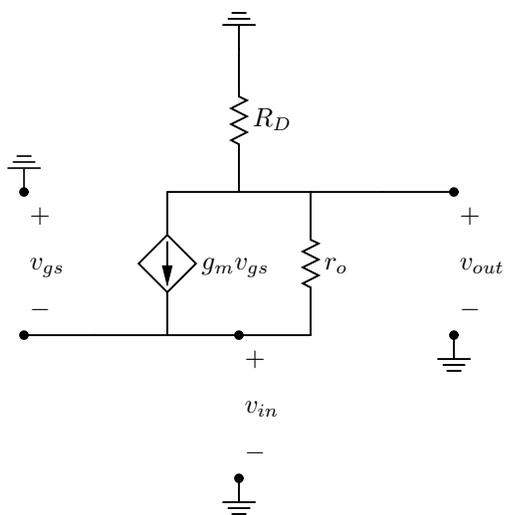

$$\begin{aligned} \frac{v_{out}}{R_D} &= g_m v_{in} + \left(\frac{v_{in} - v_{out}}{r_o} \right) \\ v_{out} \left(\frac{1}{R_D} + \frac{1}{r_o} \right) &= v_{in} \left(g_m + \frac{1}{r_o} \right) \\ A_v = \frac{v_{out}}{v_{in}} &= \frac{g_m + \frac{1}{r_o}}{\frac{1}{R_D} + \frac{1}{r_o}} \\ &= \boxed{g_m (r_o \parallel R_D) + \frac{r_o \parallel R_D}{r_o}} \end{aligned}$$