CS61C
Finishing the Datapath:
Subtract, Multiple, Divide

Lecture 21

April 14, 1999

Dave Patterson
(http.cs.berkeley.edu/~patterson)

www-inst.eecs.berkeley.edu/~cs61c/schedule.html

Outline

- Review Datapath, ALU
- Including subtract in a 32-bit ALU
- Review Binary Multiplication
- Administrivia, "What's this Stuff Good For"
- Multiplier
- Review Binary Division
- Divider
- Conclusion

Review 1/5: Steps in Executing MIPS Subset

1) Fetch Instruction and Increment PC

2) Read 1 or 2 Registers

3) Mem-ref: Calculate Address
   Arith-log: Perform Operation
   Branch: Compare if operands ==

4) Load: Read Data from Memory
   Store: Write Data to Memory
   Arith-og: Write Result to Register
   Branch: if operands ==, Change PC

5) Load: Write Data to Register

Review 2/5 : A Datapath for MIPS

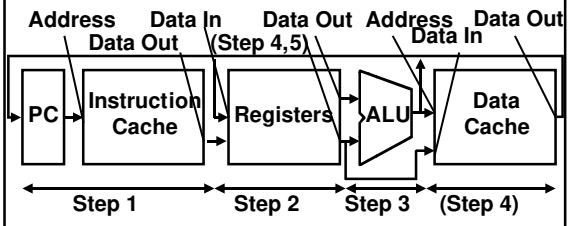

Review 3/5: Hardware Building Blocks

AND Gate

Symbol: A, B → C

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

OR Gate

Symbol: A, B → C

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Inverter

Symbol: A → C

A	C
0	1
1	0

Multiplexor

Symbol: D, A, B → 0/1 → C

D	C
0	A
1	B

Review 4/5: Add 1-bit Adder to 1-bit ALU

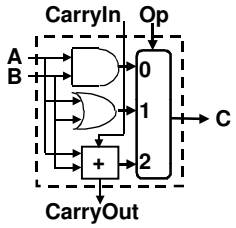

Definition

Op	C
0	A and B
1	A or B
2	A + B + CarryIn

- Now connect 32 1-bit ALUs together

Review 5/5: 32-bit ALU

- Connect $CarryOut_i$ to $CarryIn_{i+1}$
- Connect 32 1-bit ALUs together
- Connect Op to all 32 bits of ALU
- Does 32-bit And, Or, Add
- What about subtract?

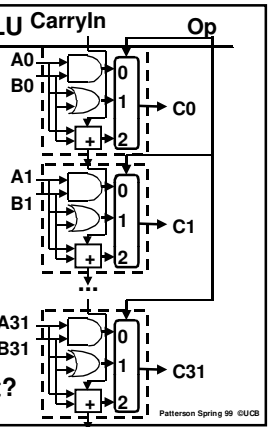

2's comp. shortcut: Negation (Lecture 7)

- Invert every 0 to 1 and every 1 to 0, then add 1 to the result
  - Sum of number and its inverted rep. ("one's complement") must be $111...111_{two}$
  - $111...111_{two} = -1_{ten}$
  - Let $\overline{x}$ mean the inverted representation of x
  - Then $x + \overline{x} = -1 \Rightarrow x + \overline{x} + 1 = 0 \Rightarrow \overline{x} + 1 = -x$
- Example: -4 to +4 to -4

x : 1111 1111 1111 1111 1111 1111 1111 1100_{two}
$\overline{x}$: 0000 0000 0000 0000 0000 0000 0000 0011_{two}
+1: 0000 0000 0000 0000 0000 0000 0000 0100_{two}
$\overline{()}$: 1111 1111 1111 1111 1111 1111 1111 1011_{two}
+1: 1111 1111 1111 1111 1111 1111 1111 1100_{two}

How Do Subtract?

- Suppose added input to 1-bit ALU that gave the one's complement of B
- What happens if set CarryIn0 to 1 in 32-bit ALU?
  - 32-bit Sum = A + B + 1
- Then if select one's complement of B ($\overline{B}$), Sum is $A + \overline{B} + 1 = A + (\overline{B} + 1) = A + (-B) = A - B$
- If modify 1-bit ALU, can do Subtract as well as And, Or, Add

1-bit ALU with Subtract Support

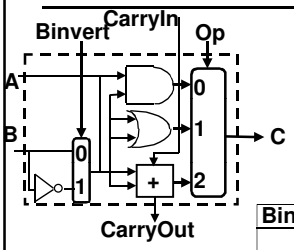

Definition

Binvert	Op	C
0	0	A and B
1	0	A and $\overline{B}$
0	1	A or B
1	1	A or $\overline{B}$
0	1	A + B + CarryIn
1	1	A + $\overline{B}$ + CarryIn

32-bit ALU

- 32-bit ALU made from AND gates, OR gates, Inverters, Multiplexors
- Performs 32-bit AND, OR,Add, Sub (2's complement)
- Op, Binvert, CarryIn are control lines; control datapath

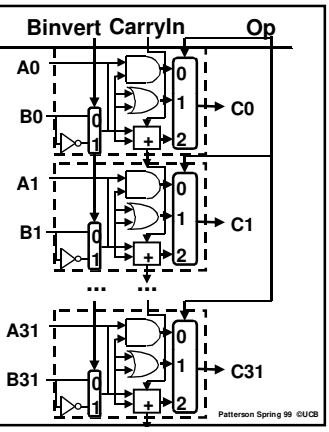

MULTIPLY: From Lecture 9

- Paper and pencil example:

```
Multiplicand 1000
Multiplier   1001
              1000
             0000
            0000
           1000
Product  01001000
```

  - m bits x n bits = m+n bit product
- MIPS: `mul`, `mulu` puts product in pair of new registers `hi`, `lo`; copy by `mfhi`, `mflo`
  - 32-bit integer result in `lo`

MULTIPLY

- Binary multiplication is easy:
  - 0 ⇒ place 0 (0 x multiplicand)
  - 1 ⇒ place a copy (1 x multiplicand)
  - Shift the multiplicand left before adding to product
- 3 versions of multiply hardware & algorithm:
  - Successive refinement to get to real version
  - Go into first version in detail, give idea of others

Shift-add multiplier (version 1)

```
1000
1001
1000
0000
0000
1000
01001000
```

64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit Multiplier reg

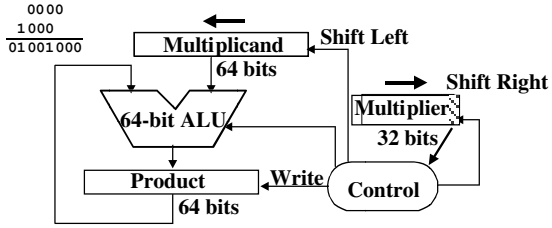

Multiplier = datapath + control

Shift-Add Multiply Algorithm V. 1

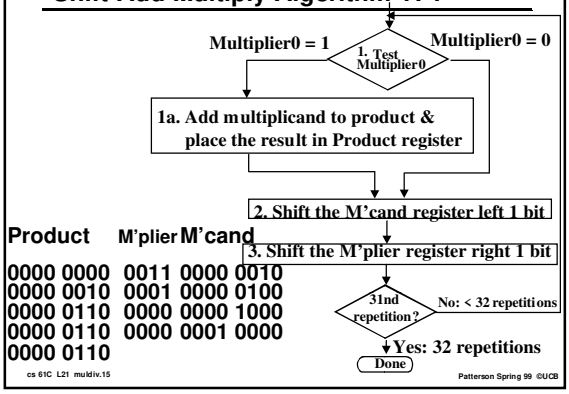

Product	M'plier	M'cand
0000 0000	0011	0000 0010
0000 0010	0001	0000 0100
0000 0110	0000	0000 1000
0000 0110	0000	0001 0000
0000 0110		

Administrivia

- Project 5: Due today
- Next Readings: 3.12, 4.9
  - Optional: Appendix D "An Alternative to RISC: the Intel 80x86," Computer Architecture, A Quantitative Approach, 2/e
  - Optional: RISC Survey (including HP ISA) ftp://mkp.com/COD2e/Web_Extensions/survey.htm
- 9th homework: Due Friday (Ex. 7.35, 4.24)
- 10th homework: Due Wednesday 4/21 7PM
  - Exercises 4.43, 3.17 (assume each instruction takes 1 clock cycle, performance = no. instructions executed * clock cycle time, ignore CPI comment)

Administrivia: Rest of 61C

F 4/16 Intel x86, HP instruction sets; 3.12, 4.9

W 4/21 Performance; Reading sections 2.1-2.5
F 4/23 Review: Procedures, Variable Args
(Due: x86/HP ISA lab, homework 10)

W 4/28 Processor Pipelining; section 6.1
F 4/30 Review: Caches/TLB/VM; section 7.5
(Due: Project 6-sprintf in MIPS, homework 11)

M 5/3 Deadline to correct your grade record

W 5/5 Review: Interrupts/Polling
F 5/7 61C Summary / Your Cal heritage

Sun 5/9 Final Review starting 2PM (1 Pimintel)

W 5/12 Final (5PM 1 Pimintel); mds@cory

"What's This Stuff Good For?"

Aquanex system
Swimmers looking for an edge over the competition can now use tiny half-ounce sensors that give them instant feedback on their power and their stroke rate, length and velocity, shown as real-time performance graphs generated by the PC. Unlike most, this swimmer generates more arm power in his butterfly than in his freestyle. "If he learns to apply that strength to his freestyle, he'll almost certainly decrease his time."
One Digital Day, 1998
www.intel.com/onedigitalday

Will computers help us utilize untapped physical potential as well as intellectual potential?

Observations on Shift-Add Multiply V.1

- 1/2 bits in multiplicand always 0 => 64-bit adder is wasted
- 0's inserted in left of multiplicand as shifted => least significant bits of product never changed once formed
- Instead of shifting multiplicand to left, shift product to right?

Shift-add Multiplier Version 2 (v. slide 14)

- 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, 32-bit Multiplier reg

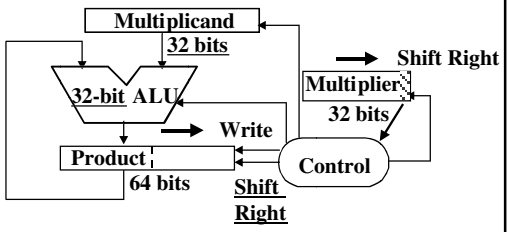

Multiplier = datapath + control

Shift-Add Multiplier Version 3

- Product reg. wastes space that exactly matches size of Multiplier reg
  ⇒ combine Multiplier reg and Product reg
  ⇒ "0-bit" Multiplier reg

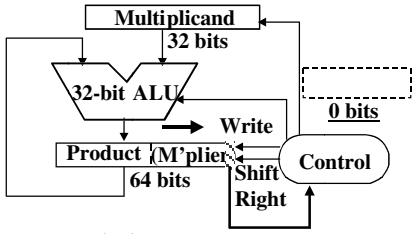

Multiplier = datapath + control

Divide: From Lecture 9

```
                  1001   Quotient
Divisor 1000 | 1001010 Dividend
             -1000
                10
                101
                1010
               -1000
                  10   Remainder
                (or Modulo result)
```

Dividend = Quotient x Divisor + Remainder

- See how big a number can be subtracted, creating quotient bit on each step
  - Binary ⇒ 1 * divisor or 0 * divisor

DIVIDE HARDWARE Version 1

64-bit Divisor reg, 64-bit ALU, 64-bit Remainder reg, 32-bit Quotient reg

```
          1001
1000 | 1001010
      -1000
         10
         101
         1010
        -1000
          10
```

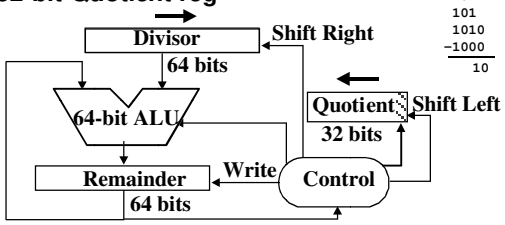

- Put Dividend into Remainder to start, collect Quotient 1 bit at a time

Divide Algorithm V. 1

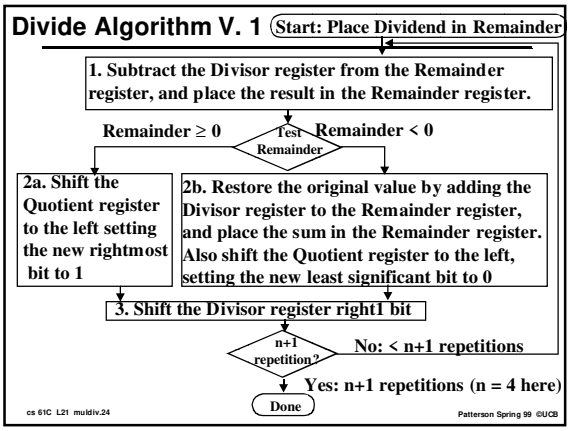

Example Divide Algorithm V. 1

- Takes n+1 steps for n-bit Quotient & Rem.

	Remainder	Quotient	Divisor	(-Divisor)
	0000 0111	0000	0010 0000	(1110 0000)
1	1110 0111			
2b		0000		
3	0000 0111		0001 0000	(1111 0000)
1	1111 0111			
2b		0000		
3	0000 0111		0000 1000	(1111 1000)
1	1111 1111			
2b		0000		
3	0000 0111		0000 0100	(1111 1100)

Example Divide Algorithm V. 1 (cont'd)

	Remainder	Quotient	Divisor	(-Divisor)
	0000 0111	0000	0000 0100	(1111 1100)
1	0000 0011			
2a		0001		
3	0000 0011		0000 0010	(1111 1110)
1	0000 0001			
2a		0011		
3	0000 0001		0000 0001	(1111 1111)

- Original division of 0111_{two} (7) by 0010_{two} (2) gives a quotient of 0011_{two} (3) plus a remainder of 0001_{two} (1)

Observations on Divide Version 1

- 1/2 bits in divisor always 0
  => 1/2 of 64-bit adder is wasted
  => 1/2 of divisor is wasted
- Instead of shifting Divisor to right, shift Remainder to left?

DIVIDE HARDWARE Version 2 (v. slide 28)

- 32-bit Divisor reg, 32-bit ALU, 64-bit Remainder reg, 32-bit Quotient reg

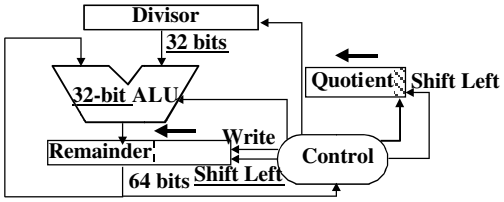

DIVIDE HARDWARE Version 3

- Eliminate Quotient register by combining with Remainder as shifted left 32-bit
  ⇒"0-bit" Quotient reg

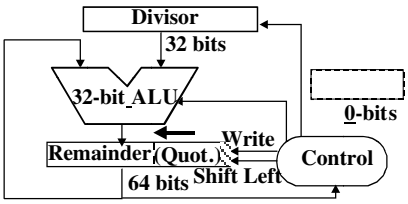

Multiply, Divide Algorithms Explain MIPS

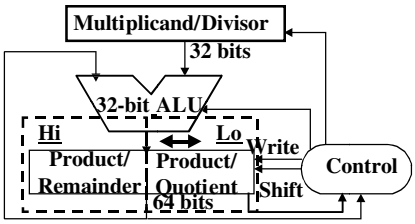

- `mul` puts product in pair of regs `hi`, `lo`;
  - 32-bit integer result in `lo`
- MIPS: `div`, `divu` puts Remainer into `hi`, puts Quotient into `lo`

A Revised Datapath for MIPS

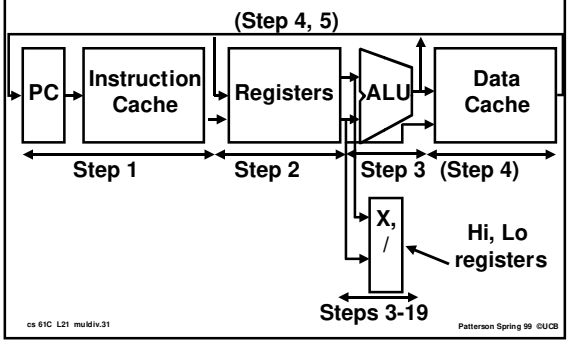

"And in Conclusion.." 1/1

- Subtract included to ALU by adding one's complement of B
- Multiple by shift and add
- Divide by shift and subtract, then restore by add if didn't fit
- Can Multiply, Divide simply by adding 64-bit shift register to ALU
- MIPS allows multiply, divide in parallel with ALU operations
- Next: Intel and HP Instruction Set Architectures